

LAB: Complex Linked State Machines in VHDL

Bill of Materials (optional task only):

DE-0 Nano FPGA Board

Female-to-female ribbon connector (JP1)

STM32F429FZ Nucleo Board

Prototyping Wires (5 off)

Software Required

Quartus Prime v16.1

Keil uVision 5.2x (Advanced task only)

PuTTY (Advanced task only)

Document Revision

V1.0 – 08/02/2018 – Initial version for ELEC241

V1.01 – 08/02/2018 – Clarified task in 01-01 to address misunderstandings in the lab

Task 01-01 Build and Test a Timer

This task is **related** to the example given in the lecture, but not exactly the same.

Problem Statement

A user presses and holds down a button x

- If the user holds down the button for 256 clock cycles (0.25s), the output Y is set to 1
- If the user releases the button before 256 clock cycles are done, the process has to start again

This task is broken down into two state machines, which are linked together (see Figure 3). The first is a reusable timer component. The second is a state machine to receive input from a switch.

In this section, you should address the first task, which is to build the timer sub-component in VHDL. The ASM chart for the timer is shown in Figure 1.

 


Figure 1. ASM Chart for the Timer

To get you started, a template project has been provided (LinkedFSM.zip). The VHDL entity and architecture have been provided. The entity is also shown below.

```
entity counter_233 is
    port(
        clk      : in std_logic;
        start    : in std_logic;
        reset     : in std_logic;

        ready    : out      std_logic
    );
end entity;
```

However, the architecture is not yet complete. Below is the beginning of the architecture that is yet to fully conform to the design in Figure 1.

TASKS

1. Complete the Timer architecture below. Note the comments indicating where you need to write more code. Follow the ASM chart carefully.
2. Create a symbol for this component and place it on the top-level schematic. Add some inputs and outputs for test purposes.
3. Build the code.
4. Create vector waveform file to test this device. Think carefully about what test inputs will verify the design in the ASM chart (assessed).
5. Show your solution and test results in your log book.

Tips:

Use `if-elsif-else` instead of a `case` statement.

States S0 to S254 are identical. They only need a single `if` statement.

Question: If we modify the number of states to count from S0 to S254, how many gates / registers do we save? Comment on the reason for the difference.

```
architecture rtl of counter_233 is
    signal state : integer range 0 to 256 := 0;
begin
    -- Logic to advance to the next state
    process (clk, reset)
    begin
        if (rising_edge(clk)) then
            if (state = 0) then
                if (start = '1') then
                    state <= 1;
                end if;

                -- ***** TO BE DONE *****

            end if;
        end if;
    end process;

    -- Output depends solely on the current state
    process (state)
    begin
        -- **** TO BE DONE ****
    end process;
end rtl;
```

Task 01-02 Linking the Switch Controller to the Timer with the Schematic Editor

Now you need to build a second component. This is left hand ASM chart in Figure 2. The component on the right is the timer component from the previous task. The dashed lines represent the connections between the two components.

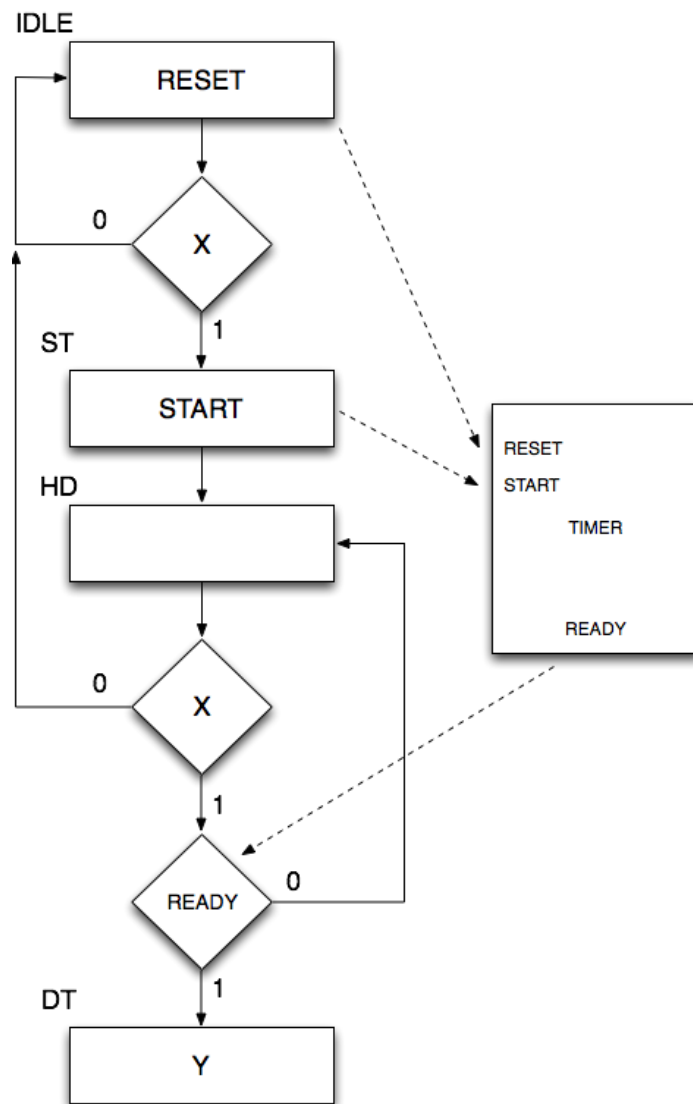


Figure 2. ASM Chart for a switch controller. This system has three outputs (RESET, START and Y) and two inputs (X and READY)

Once again, you are provided with the entity, and only part of the architecture.

Complexed Linked State Machines

```
entity control_button is
    port(
        clk          : in std_logic;
        X            : in std_logic;          --Switch input
        timer_ready   : in std_logic;         --Timer is ready input

        --Outputs
        reset_timer   : out std_logic;
        start_timer   : out std_logic;
        Y             : out std_logic
    );
end entity;
```

For the architecture shown below, the more standard case-statement based state machine is used. However, it is not complete.

TASKS

1. Complete the architecture below. Note the comments indicating where you need to write more code.
2. Create a symbol for this component and place it on the top-level schematic. Add some inputs and outputs for test purposes.
3. Connect to the timer component
4. Build the code.
5. Create vector waveform file to test this device. Think carefully about what test inputs will verify the design in the ASM chart (assessed) and the design brief.
6. Show your solution and test results in your log book.

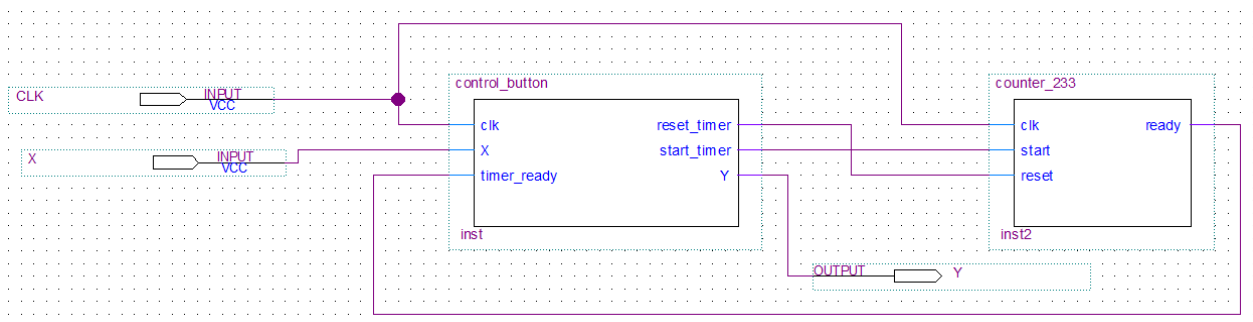


Figure 3. Showing the coupling of two state machines using the schematic editor

Question: Comment on why we have split the design into two state machines. What are the benefits?

```

architecture rtl of control_button is
    -- Build an enumerated type for the state machine
    type state_type is (IDLE, ST, HD, DT);
    signal state : state_type := IDLE;
begin

    process (clk) -- Logic to advance to the next state
    begin
        if (rising_edge(clk)) then
            case state is
                when IDLE=>
                    if X = '1' then
                        state <= ST;
                    else
                        state <= IDLE;
                    end if;
                when ST=>
                    -- **** To be done ****
                when HD=>
                    -- **** To be done ****
                when DT =>
                    -- **** To be done ****
            end case;
        end if;
    end process;

    process (state) -- Output depends solely on the current state
    begin
        case state is
            when IDLE =>
                Y <= '0';
                -- **** To be done ****
            when ST =>
                -- **** To be done ****
            when HD =>
                -- **** To be done ****
            when DT =>
                -- **** To be done ****
        end case;
    end process;
end rtl;

```

Task 01-03 Linking the Switch Controller to the Timer with Structural VHDL


In the previous task, two state machines were linked by simply wiring them together in a schematic. However, what if we didn't use a schematic, or maybe wanted to create another VHDL entity that combined them together?

1. Refer to the previous module where we covered **structural VHDL**.
2. Now create a third entity in VHDL called `button_hold` as shown below
3. Your task is to create the architecture and use structural VHDL to import and connect both the timer and the switch controller.
4. You should then create a symbol for this component and place it on the top level schematic.
5. You should now test this new component to show it produces the same output as in the previous section.

```
entity button_hold is
    port(
        clk          : in std_logic;
        X             : in std_logic;      --Switch input

        --Outputs
        Y             : out std_logic
    );
end entity;
```

Really useful TIP: Use the template generator in Quartus to help you! While editing your VHDL code, right click and select insert template. Choose VHDL->Constructs. Look for “Component Declaration” and “Component Instantiation” (You don't need the generic sections).

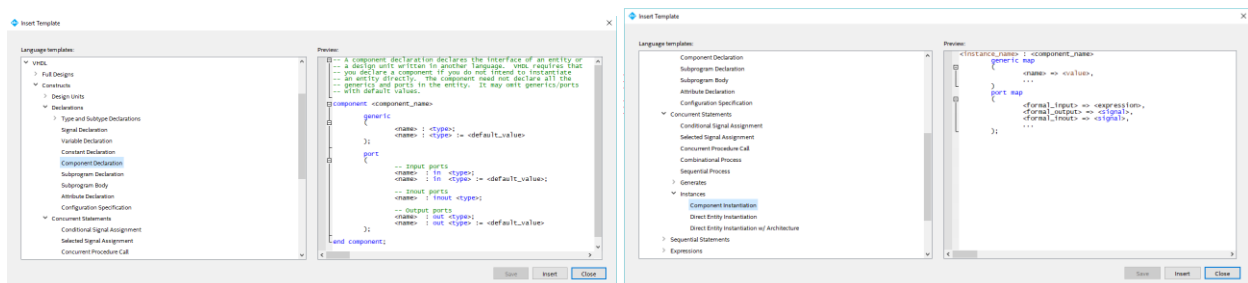

Task 02-01 Switch Debounce Component

You task is now to adapt what you did above to build a full switch debounce component. This component should have the following Entity:

```
entity switch_debounce is
    port (
        clk          : in std_logic;
        X            : in std_logic;      --Switch input

        --Outputs
        Y            : out std_logic
    );
end entity;
```

Requirements

1. The output Y should **toggle** every time the input is goes HIGH then LOW.
2. A timer should be used to add a suitable clock delay to prevent switch bounce. Assume a clock frequency of 1024Hz.

Tasks

- Draw a new ASM chart for this device. Use the existing timer as in previous tasks (you should not need to modify it)
- Create a VHDL entity `switch_debounce`. Use the entity shown above. Remember that each entity should be in a VHDL file of the same name.
- Write the architecture. For full marks, use structural VHDL to link to the timer.
- Create a symbol file for the new component
- Test the component using a vector waveform file. Again, think carefully about the input sequences. Remember to include cases where switch bounce occurs (simulate this).
- Include your ASM chart, VHDL and test results in your log book

Question: Each time you test your design, consider how long it takes check the waveform output. Comment on how this approach impacts on your productivity, how it might scale as the design becomes more complex, and how reliable this approach is.

Optional Task Connecting the FPGA to the Nucleo F429ZI Board

This task is neither assessed or ready! Please check back for a status update.

For fun, you could try connecting this device to the Nucleo Board. Set up an interrupt to output the USER_BUTTON state to a GPIO pin. This pin should then be connected to the DE-0 FPGA board.

You will need to use the phase locked loop to generate a 1024Hz clock.

1. Connect the ribbon cable to the FPGA connector JP1 as shown in Figure 4.


 
 


Figure 4. Showing the connections between the FPGA and the Nucleo Board

2. Using the connections in Table 1, connect the FPGA to the Nucleo Board using prototyping wires. Use Figure 5, Figure 6 and Figure 7 to locate the correct pins.

Table 1. Nucleo to DE0 Nano Connections for the SPI interface

MCU Signal	MCU Pin	FPGA Pin
SWITCH_OUT	PC_6 (D16)	A2 (JP1-Pin 5) GPIO_2
SWITCH_IN	PA_7 (D11)	D6 (JP1-Pin18) GPIO_13

 

 


Figure 7. Nucleo FZ429ZI


 


Figure 8. Showing the pin 1 on the FPGA DE-0 Nano Board

Rev. 1.01

Complexed Linked State Machines

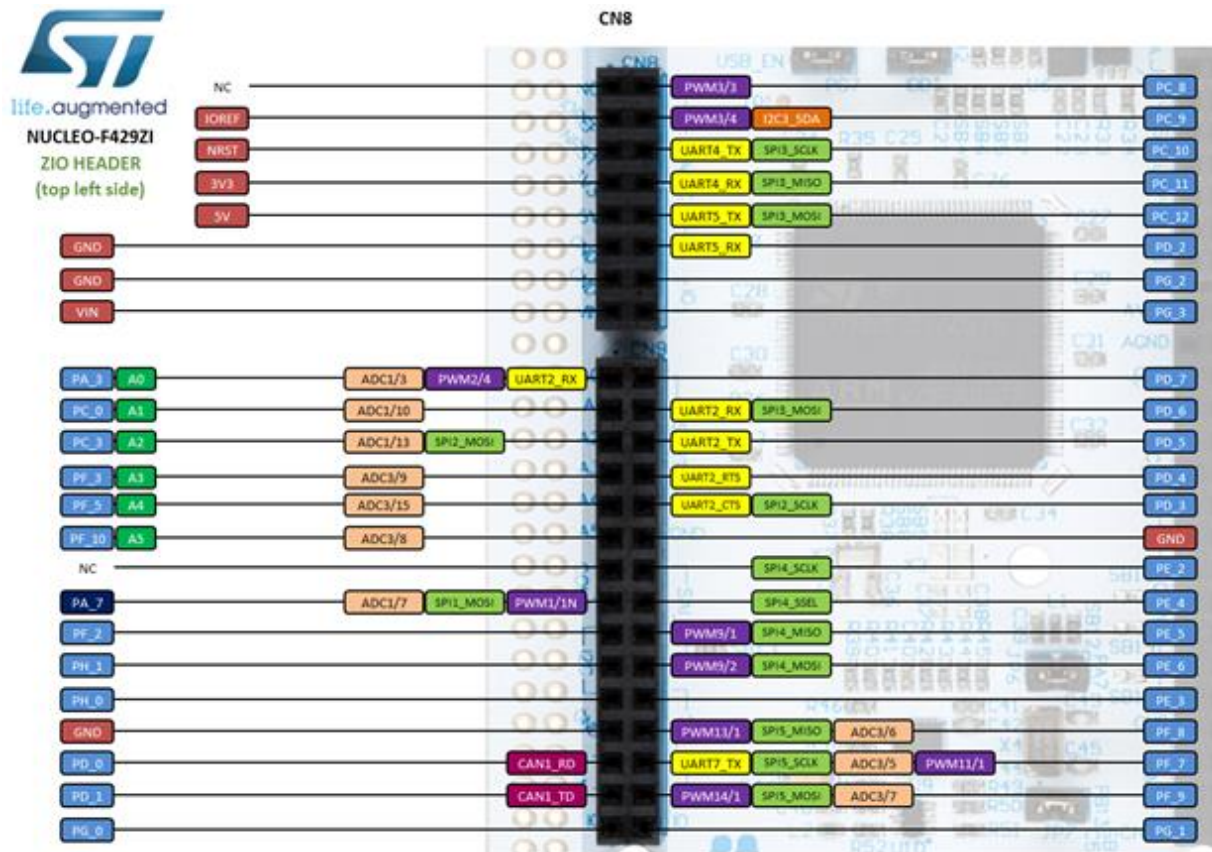

Appendix B – ASM Charts

 


Figure 10 State with Moore Output Signal. The state name and assignment (optional) area all unique

 


Figure 11 State Transition Decision. The variable Z is being tested. This must ultimately lead to a state box, possibly via another decision and/or Mealy Output(s)

 


Figure 12. Mealy Output. The example here is the START_ENGINE signal which is asserted high. It only makes sense to connect a decision symbol to the input of the Mealy output symbol.